

Roll No.

97664

**BCA 1st Semester (New)
Examination – November, 2018
LOGICAL ORGANIZATION OF COMPUTERS-I**

Paper : BCA-104

Time : Three Hours]

[Maximum Marks : 80

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *four* questions by selecting *one* question from each Unit. Question No. 1 is *compulsory*. All questions carry equal marks.

1. (a) What is BCD adder ? 2 × 8 = 16
(b) What is meant by digital logic ? Explain.
(c) What is the difference between Boolean Algebra and Real Algebra ?
(d) Which number system is followed in digital computers and why ?
(e) What are Demultiplexers ? State their importance.
(f) What is Unicode ? State its relevance.
(g) What is the smallest and largest integer number represented in a 32-bit computer ?
(h) What are code converters ?

97664-7,350-(P-3)(Q-9)(18)

P. T. O.

UNIT - I

2. (a) What are parity bits ? How are these relevant in error-detection and correction codes ? Illustrate through suitable examples. 7
- (b) Find out the values of X, Y and Z in the following : 9
- $(75.75)_{10} = (X)_2 = (Y)_8 = (Z)_{16}$
3. Explain the following :
- (a) Floating-point Representation of numbers 8
- (b) Character codes 8

UNIT - II

4. (a) What is principle of Duality ? Illustrate. 6
- (b) Simplify the following Boolean expression using K-map : 10
- $F(a,b,c) = \Sigma(1,4,5,6,7)$
- and realize the same using NAND gates.
5. Explain the following :
- (a) SOPs and POSs 5
- (b) Venn diagrams 5
- (c) Boolean Algebra 6

UNIT - III

6. (a) What are Universal Gates ? Why these are named so ? Justify. 6
- (b) Design a combinational circuit that receives 4-bit binary input and produces its 2's complement. 10

7. (a) What do you mean by multilevel NAND and NOR circuits ? Illustrate. 4
- (b) What are AND-OR-INVERT and OR-AND-INVERT implementation ? Explain. 4
- (c) What is combinational circuit ? What are its characteristics ? Detail out the procedure for design of combinational circuit. 8

UNIT - IV

8. (a) What is a multiplexer ? How does it work ? What are its applications ? Explain. 8
- (b) What is a full-adder ? Design a full-adder and implement the same using gates. 8
9. Explain the following :
- (a) BCD to seven-segment Decoder 8
- (b) Magnitude Comparators 8