

Roll No. ....

**97666**

**B.C.A. 2nd Semester**

**Examination-May, 2017**

**Logical Organisation of Computers**

**Paper-BCA-107**

**Time : 3 hours**

**Max. Marks : 80**

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard will be entertained after the examination.

**Note :** Attempt **five** questions in all. Question No.1 is **compulsory** and attempt **four** more questions by selecting **one** question from each unit. All questions carry equal marks.

**1.** Compulsory questions [8×2]

(a) What is clocked RS flip-flop ?

(b) Why Master-Slave flip-flop is called so ?

(c) What is up-down counter ?

7. Explain the follow:

(a) Magnetic Disl [8]

(b) Characteristic Memory Cell [8]

UN /

8. (a) What are Int pts ? How are these useful ? What interrupt structure ? Illustrate. [8]

(b) What are I/O nels ? How do these work ? Illustrate their working. [8]

9. Explain the followi

(a) Instruction Fe [8]

(b) Instruction Cy [8]

<https://www.ndupapers.com>

- (d) What is an Instruction Format ?
- (e) What are applications of ROM ?
- (f) What is a parallel-controlled I/O technique ?
- (g) What is an IOP and its significance.
- (h) What characterizes Flash Memory ?

### UNIT-II

- 2. (a) What are Excitation Tables ? How are these relevant ? Draw Excitation Table for RS and JK flip-flops. [8]
- (b) What are State Transition Diagrams ? How are these relevant in design of Flip-flops ? Explain. [8]
- 3. Explain the following:
  - (a) Master-Slave Flip-flop [8]
  - (b) T Flip-flop [8]

https://www.ndupapers.com

### UNIT-II

- 4. (a) What are Synchronous Binary Counters ? Draw its block diagram and illustrate its operation. [8]
- (b) What are the general characteristics of good shift registers ? Design a 4-bit shift register and outline the procedure for serial to parallel conversion and vice-versa. [8]
- 5. Explain the following:
  - (a) Asynchronous Sequential Circuit [8]
  - (b) Modulo-5 Counter [8]

### UNIT-III

- 6. (a) What are I/O Device Controllers ? How do these work ? Illustrate their working. [8]
- (b) What is Semiconductor RAM ? How do you design a RAM cell ? Illustrate. [8]