

**24004**

**B. Tech. 1st Semester F-Scheme Examination,**

**December-2014**

**BASICS OF ELECTRONICS**

**Paper-ECE-101-F**

*Time allowed : 3 hours]*

*[Maximum marks : 100*

---

*Note : (1) Attempt a total of five questions.*

*(2) Question No. 1 is compulsory. One question to be attempted from each unit.*

*(3) The sub parts of questions should be attempted together only.*

- |        |   |   |
|--------|---|---|
| 1. (a) | Explain conditions for oscillation.             | 2 |
| (b)    | Characteristics of Ideal Op Amp.                | 3 |
| (c)    | Define flip flops and their purpose.            | 4 |
| (d)    | Difference between Diffusion and Drift current. | 4 |
| (e)    | Difference between ON-line and OFF line UPS.    | 4 |
| (f)    | Applications of seven segment display.          | 3 |

**Unit-I**

2. Draw the diagram of P N junction and explain its behaviour in : 20
- (a) Open circuit.

- (b) Forward bias.
- (c) Reverse bias.
3. (a) Draw the circuit diagram of RC coupled amplifier and explain its working principle and frequency response. 15
- (b) Why negative feedback is essential for amplifiers ? 5

### Unit-II

4. (a) Explain working of crystal oscillator. 10
- (b) Explain briefly Applications of Op Amp. 10
5. (a) Explain working of voltage regulators and their applications. 10
- (b) Describe working principle of Inverter and its applications. 10

### Unit-III

6. (a) Convert the following : 10
- (i)  $(8AB4.01)_{16}$  into Octal.
- (ii)  $(754.32)_8$  into Decimal.
- (iii)  $(1094.45)_{10}$  into Hexadecimal.
- (iv)  $(10111001100)$  into Decimal.

( 3 )

**24004**

(b) Realize all basic gates using NAND gates. Also write the truth table. 10

7. Write short notes on : 10×2

(a) Digital Multi meter

(b) Signal generator.

#### **Unit-IV**

8. (a) Draw the diagram of seven segment display and write the truth table. 10

(b) Explain working of Dynamic scattering type LCD display. 10

9. Write short notes on : 10×2

(a) Working principle and advantages of LED.

(b) Advantages and disadvantages of LCD display.