

Roll No.

24004

**B. Tech. 1st Sem. (Common for All
Branches) Examination – December, 2018**

BASICS OF ELECTRONICS

Paper : ECE-101-F

Time : Three Hours]

[Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *five* questions in all, selecting *one* question from each Section. Question No. 1 is *compulsory*.

1. Write short notes on the following : 20

- (a) Amplifiers
- (b) LED
- (c) UPS
- (d) CRD

24004-2,350-(P-3)(Q-9)(18)

P. T. O.

SECTION – A

2. (a) Explain P-N junction is the breakdown region. 10
(b) Describe terminal characteristics of junction diode. 10
3. (a) Describe Frequency response of RC coupled Amplifier. 10
(b) Discuss working of Cascaded Amplifier. 10

SECTION – B

4. (a) What is criteria of oscillations ? Explain. 10
(b) Explain working of SMPS. 10
5. Explain different characteristics and applications of op-amps. 20

SECTION – C

6. (a) Explain SR and J-K flip flop. 10
(b) Derive various gates using universal gates. 10
7. (a) Describe working of function generator. 10
(b) Compare analog and digital multimeter. 10

24004-2,350-(P-3)(Q-9)(18) (2)

SECTION – D

8. Describe construction and working of LED in detail. 20
9. (a) What is dot matrix display. Explain. 10
(b) What is seven segment display. Explain. 10

24004-2,350-(P-3)(Q-9)(18) (3)