

Roll No. ....

**24004**

**B. Tech. 1st Semester**

**Examination – December, 2013**

**BASICS OF ELECTRONICS**

'F' Scheme

Paper : ECE-101-F

*Time : Three hours ]*

*[ Maximum Marks : 100*

*Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

*Note : Attempt five questions in all, selecting one question from each Section Question No. 1 is compulsory.*

1. (a) Explain the necessity of doping. 2
- (b) Why is silicon more widely used for semiconductor material ? 2
- (c) What is positive feedback ? Where is it used ? 2
- (d) What is slew rate ? 2

- (e) What is Race-around condition ? 3
- (f) Why is the efficiency of SMPS high ? 3
- (g) Convert  $(FF3B)_{16}$  to equivalent decimal. 3
- (h) What is the function of "delay line" in an oscilloscope ? 3

### SECTION - A

2. (a) What is meant by biasing of a p-n junction diode ?  
Why is it necessary ? Also explain the V-I characteristics of junction diode. 10
- (b) Explain R-C coupled amplifier draw its frequency response curve at different frequencies. 10
3. (a) Explain the concept of cascaded amplifier. Why cascading is required ? 10
- (b) Discuss the advantages and disadvantages of

### SECTION - B

4. (a) What is crystal oscillator ? Draw its equivalent circuit and derive result for impedance and resonant frequency. 10
- (b) Explain the block diagram of Op-amp. 10
5. (a) Compare the working of Inverter and UPS. 10
- (b) Explain voltage regulator with the help of block diagram. 10

### SECTION - C

6. (a) What are universal gates ? Realize all the gates using universal gates. 10
- (b) Explain the working of J-K flipflop. 10
7. (a) Discuss role, importance and application of test instruments. 10
- (b) Explain the working of function generator. 10

### SECTION - D

8. (a) Explain the type of liquid crystal cells. 10

(b) Discuss the advantages and disadvantages of LCD display. 10

9. (a) How fourteen segment display works ? Design a circuit for it. 10

(b) What is LED ? Why LED's emit light of different colours ? Give its advantages and disadvantages. 10

---